 


COA Lab Evaluation I - Set I

1. For the circuit given below, draw the full truth table (two inputs, 5 outputs) and full logic equation in a sheet of paper and conclude which logic gate the circuit resembles. Design the *data flow Verilog HDL* for the full circuit in your system. [10 marks]



2. For the logic equation given below, draw the full truth table and circuit diagram in a sheet of paper and conclude which logic gate the circuit resembles. Design the *data flow Verilog HDL* for the full circuit in your system.

$$\{ [A \text{ NOR } (A \text{ NOR } B)] \text{ NOR } [B \text{ NOR } (A \text{ NOR } B)] \} \text{ NOR } \{ [A \text{ NOR } (A \text{ NOR } B)] \text{ NOR } [B \text{ NOR } (A \text{ NOR } B)] \}$$

COA Lab Evaluation I - Set II

1. For the logic equation given below, draw the full truth table and circuit diagram in a sheet of paper and conclude which logic gate the circuit resembles. Design the *data flow Verilog HDL* for the full circuit in your system. [10 marks]

$$\{ [A \text{ NAND } (A \text{ NAND } B)] \text{ NAND } [B \text{ NAND } (A \text{ NAND } B)] \} \text{ NAND } \{ [A \text{ NAND } (A \text{ NAND } B)] \text{ NAND } [B \text{ NAND } (A \text{ NAND } B)] \}$$

2. For the circuit given below, draw the full truth table (two inputs, 5 outputs) and full logic equation in a sheet of paper and conclude which logic gate the circuit resembles. Design the *data flow Verilog HDL* for the full circuit in your system. [10 marks]

